

Contents

Week 3 : Understand the JTAGG interface perfectly	1
JTAGG interface	1
Inputs	1
Outputs	1
Concrete Logic behind Outputs :	1
TAP controller	3
How does it works ?	4
Example of usage	4
Questions	5

Week 3 : Understand the JTAGG interface perfectly

JTAGG interface

Inputs


1. **JTDO1**: If ER1 instruction is shifted into the JTAG instruction register, TDO output will come from JTDO1.
2. **JTDO2**: If ER2 instruction is shifted into the JTAG instruction register, TDO output will come from JTDO2.
3. **TCK***: Clock used to clock the registers and the TAP controller, *connected to the actual JATG pins*
4. **TMS***: Control states machine witching for TAP controller, *connected to the actual JATG pins*
5. **TDI***: Test Data input, *connected to the actual JATG pins*

Outputs

1. **TDO***: Test Data Output, *connected to the actual JATG pins*
2. **JTCK**: Signal coming from TCK and going to the FPGA logic (the internal clock)
3. **JTDI**: Coming from the TDI and connected to the FPGA logic
4. **JRTI1**: If ER1 instruction is shifted into the JTAG instruction register, JRTI1 will go high when TAP controller is in Run-Test/Idle state.
5. **JRTI2**: If ER2 instruction is shifted into the JTAG instruction register, JRTI2 will go high when TAP controller is in Run-Test/Idle state.
6. **JSHIFT**: Goes high when the TAP controller is in the state SHIFT-DR
7. **JUPDATE**: Goes high when the TAP controller is in the state UPDATE-DR
8. **JRSNT**: (*Active low*) goes low when in the state TEST-LOGIC-RESET
9. **JCE1**: If ER1 instruction is shifted into the JTAG instruction register, JCE1 will go high when TAP controller is in Capture-DR or Shift-DR states.
10. **JCE2**: If ER2 instruction is shifted into the JTAG instruction register, JCE2 will go high when TAP controller is in Capture-DR or Shift-DR states.

Concrete Logic behind Outputs :

1. TDO is **z** if not in a shift state, else **ir_shadow_reg[0]** if in shift_ir, else JTDOx if in shift_dr state with x corresponding to the instruction in the ir_shadow_reg
2. JTCK = TCK
3. JTDI = TDI on posedge of TCK
4. JRTI1 = run_test_idle && (ir_shadow_reg == 8'h32)
5. JRTI2 = run_test_idle && (ir_shadow_reg == 8'h38)
6. JSHIFT = shift_dr && (ir_shadow_reg == 8'h32 || ir_shadow_reg == 8'h38)
7. JUPDATE = update_dr && (ir_shadow_reg == 8'h32 || ir_shadow_reg == 8'h38)
8. JRSNT = !test_logic_reset
9. JCE1 = (capture_dr || shift_dr) && (ir_shadow_reg == 8'h32)

 

INPUTS: TCK, TMS, TDI, JTDO2, JTDO1

OUTPUTS: TDO, JTDI, JTCK, JRTI2, JRTI1, JSHIFT, JUPDATE, JRSTN, JCE2, JCE1

Description

The JTAGG element is used to provide access to internal JTAG signals from within the FPGA fabric. This element is used for some cores, such as Reveal Logic Analyzer, and other purposes. Most users would typically not use this component directly.

Figure 1: JTAGG interface

10. JCE2 = (capture_dr || shift_dr) && (ir_shadow_reg == 8'h38)

TAP controller

The logic controller of this interface is the standart JTAG TAP :

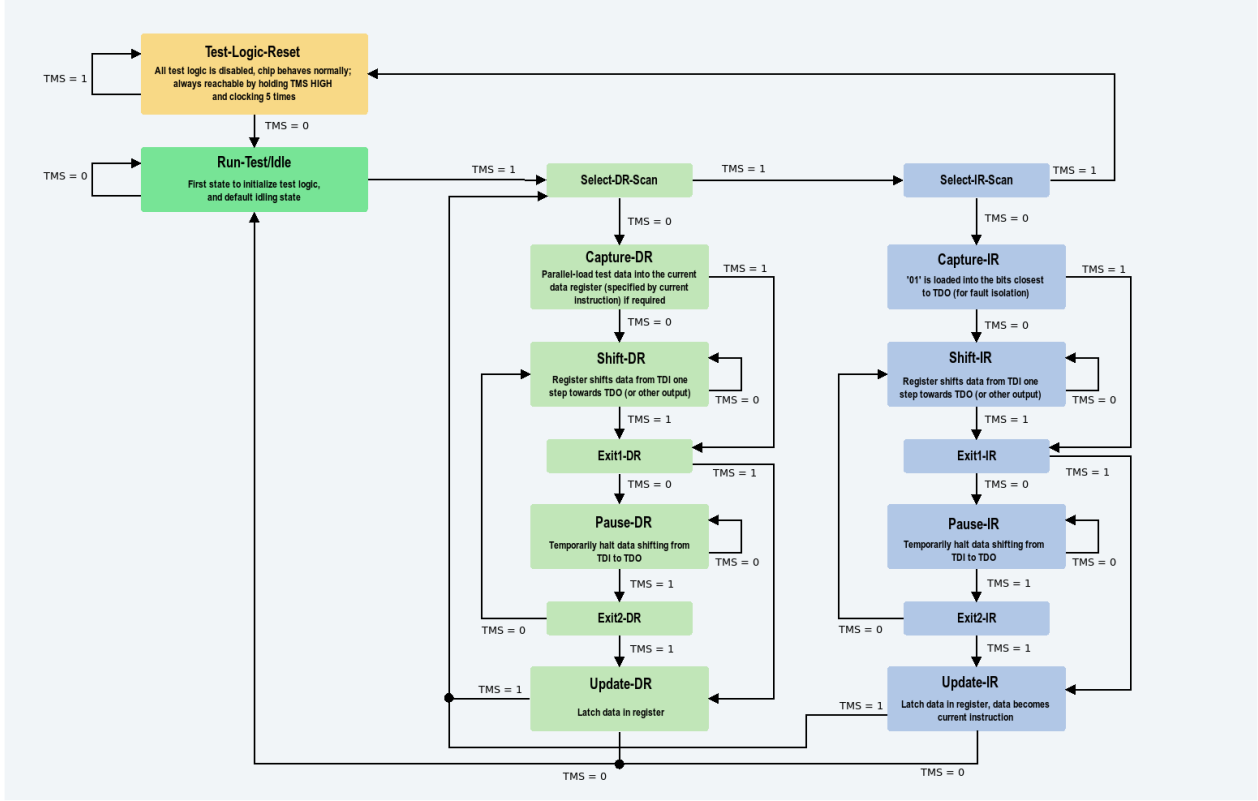


Figure 2: JTAGG TAP

JTAG TAP State Machine

General States

- **Test-Logic-Reset:** Resets all test logic, making the chip behave normally. Always reachable by holding TMS HIGH and clocking five times.
- **Run-Test/Idle:** Default state for initializing test logic; used when no scanning is happening.

Data Register (DR) Path

- **Select-DR-Scan:** Entry point for DR operations.
- **Capture-DR:** Loads test data into the currently selected data register.
- **Shift-DR:** Moves data serially from TDI to TDO one step per clock cycle.
- **Exit1-DR:** Temporary exit before either pausing or updating DR.
- **Pause-DR:** Temporarily stops shifting without losing data.
- **Exit2-DR:** Option to return to shifting or proceed to updating DR.
- **Update-DR:** Latches shifted data into the register.

Instruction Register (IR) Path

- **Select-IR-Scan:** Entry point for IR operations.

- **Capture-IR:** Loads predefined bits (“01”) for fault isolation.
- **Shift-IR:** Moves instruction data serially from TDI to TDO one step per clock cycle.
- **Exit1-IR:** Temporary exit before either pausing or updating IR.
- **Pause-IR:** Temporarily stops shifting without losing data.
- **Exit2-IR:** Option to return to shifting or proceed to updating IR.
- **Update-IR:** Latches shifted instruction into the register, making it the active instruction.

Inputs/Outputs Inputs:

- **TCK**
- **TMS** : Controls the transitions
- **TDI** : Not used

Outputs:

- **Test_logic_reset:** True when in the Test_logic_reset state
- **Run_Test_idle:** True when in the Run_test_idle state
- **Capture_dr:** “”
- **Shift_dr:** “”
- **Update_dr:** “”
- **Capture_ir:** “”
- **Shift_ir:** “”
- **Update_ir:** “”

Concrete Example of how it's working : [TAP example1](#) [TAP example 2](#)

How does it works ?

The JTAGG interface supports two instructions :

1. **ER1:** 0x32 (0b110010)
2. **ER2:** 0x38 (0b111000)

Depending on the instruction choosed one of the two chain of the IP core is used

Example of usage

The idea will be to send “01100110” to the first instruction chain **h32**

1. First we need to store the **h32** in the instrucion register to select the first chain
 1. Set TMS to 1 for at least 5 clock cycles to return in the Test_Logic_Reset from anywhere in the FSM
 2. Set TMS to 0 1 1 to reach the Select-IR-Scan state and select the Instruction path (Test_logic_reset -> Run-Test/Idle -> Select-DR-SCAN -> Select-IR-Scan)
 3. Set TMS to 0 to reach the Capture_IR state, here the instruction register is shifted in the the shift instruction register (since we reset earlier it is zeroes)
 4. Shift **h32** in the shift register
 - Set TMS 0 0 0 0 0 0 0 0 to enter Shift_IR state and shift the TDI value in the 8 bits of the shift register
 - Set TDI 0 0 1 1 0 0 1 0 to put **h32** in the shift register
 5. Update the IR register with the value in the shift instruction register by setting TMS to 1 1 and reaching Update_IR state
 6. Now the **h32** instruction is loaded into the instruction register
2. Now we need to send “0110011” to the first instruction chain
 1. Set TMS to 1 to move from the Update_IR state to the Select-DR-SCAN and to select the data path
 2. Set TMS to 0 to move to the Capture_DR state (Here no register just activate outputs signal: JCE1)

3. Send “01100110” to the chain
 - Set TMS to 0 0 0 0 0 0 to enter and stay in shift_dr state, here the chain *knows* because JCE1, and JSHISHT are set high
 - Set TDI to 0 1 1 0 0 1 1 to send the value to the chain since JTDI is connected directly to TDI
4. set TMS to 1 1 to stop shifting and reaching Udate-DR (JUPDATE set high)
5. set TMS to 0 to return to the state where the process runs normally

 


Figure 3: Waves of this example

Above we have a writing example, a example from reading is trivial since we just have to listen to the **TDO** pin that is link to the JTDO of a specific instruction depending on which instruction is loaded

Questions

1. How can I find all pins of the board so that I can connect them to my designs
2. Can you show me a demonstration of how to put a circuit on the board
3. How can i debug the JTAGG interface if i don't have access to the source code ? using leds for the signals?